



5. What is the logic expression corresponding to the following truth table, in the form  $\text{Out} = f(A, B, C)$

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- a.  $\text{Out} = A.B + A.C$
- b.  $\text{Out} = A.B' + A.C$
- c.  $\text{Out} = A.B' + B.C$
- d.  $\text{Out} = A.B.C + A'.C$
- e.  $\text{Out} = A.B.C + A'.B'.C'$
- f.  **$\text{Out} = A.B + A.C + B.C$**

6. Simplify the Boolean expression:

$$a.b'.c'.d + a.b'.c.d + a.b.c'.d + a.b.c.d' + a.b.c.d$$

- a.  $a.b.c + a.b.d + b.c.d$
- b.  **$a.d + a.b.c$**
- c.  $a.c + a.b.d$
- d.  $a.c + b.d + b.c$
- e. can't be simplified

7. How many *select* lines does an 8 data input multiplexer have?

- a. 1
- b. **3**
- c. 8
- d. 64
- e. 256

8. How many *output* lines does an 8 data input multiplexer have?

- a. **1**
- b. 3
- c. 8
- d. 64
- e. 256

9. How many *inputs* does a full adder have?

- a. 1
- b. 2
- c. **3**
- d. 4
- e. It depends on the number of bits in the numbers being added

10. What logic circuit would you use for addressing memory?

- a. Full adder
- b. Multiplexer
- c. **Decoder**
- d. Multi-input and gate
- e. Direct Memory Access circuit