

Introduction to Computing Systems
from bits & gates to C & beyond

Chapter 3


Digital Logic Structures

- *Transistors*
- *Logic gates & Boolean logic*
 - *Combinational logic*
 - *Storage Elements*
 - *Memory*

Electronic ones and zeros


- **An electronic switch**

 - like a light switch or faucet
- switches between insulator (open circuit) and conductor (closed circuit)
- We can call the presence of a voltage “1” and its absence “0”



Transistors

 
- An electronic switch that is open or closed between the *source* and the *drain* depending on the voltage on the *gate*.




CMOS Transistors

• CMOS

 - = Complementary Metal-Oxide Semiconductor
- Standard type for digital applications
- Two versions: P-type (positive) and N-type (negative)
- P and N-type transistors operate in inverse modes




 Open (insulating) if gate is “on” = 1
Closed (conducting) if gate is “off” = 0



Open (insulating) if gate is “off” = 0
Closed (conducting) if gate is “on” = 1


Inverter Gate

 

In	Out
0	1
1	0


- When the input is on (in = high voltage), the P-type transistor is *open* and the N-type is *closed*, so the output is off (out = low voltage).
- Vice-versa: when the Input is off (in = low voltage), the output is connected to the high voltage.

NOR Gate

 


A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

NOR Gate - Operation

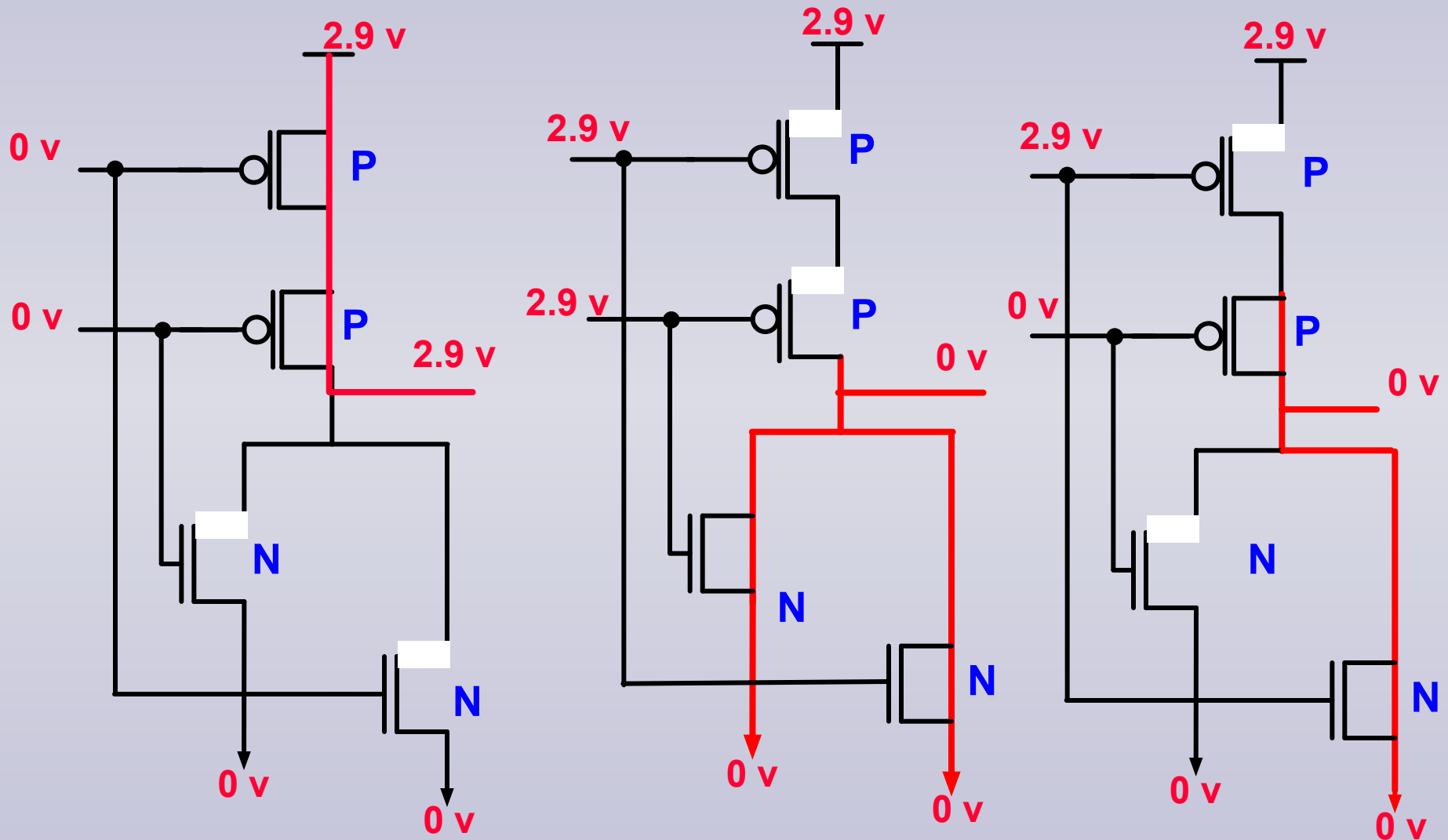


OR Gate

= a NOR gate followed by an inverter

 


A	B	C	D
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

NAND & AND Gates

 


A	B	C	D
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1


Logic Gates & Symbols

 


(a) Inverter

 


(b) AND gate

 

(c) OR gate

 

(d) NAND gate

 


(e) NOR gate

Note that gates can have more than 2 inputs.

De Morgan's Law


- **not(A and B) = (not A) or (not B)**
 
$$\overline{A \text{ and } B} = \overline{A} \text{ or } \overline{B}$$



- **not(A or B) = (not A) and (not B)**
 
$$\overline{A \text{ or } B} = \overline{A} \text{ and } \overline{B}$$




Completeness

- It can be shown that any truth table (i.e. any binary function of two variables) can be reduced to combinations of the AND & NOT functions, or of the OR & NOT functions.
 - *This result extends also to functions of more than two variables*
- In fact, it turns out to be convenient to use a basic set of three logic gates:
 - AND, OR & NOT
 - or
 - NAND, NOR & NOT

Representation of Logic Functions

 - A logic function can be represented as
 - a truth table
 - a logic expression
 - a logic circuit
- Example




a	b	c	d	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Types of Logic Structures

- Two types of logic structures ==> two types of logic circuits
 - Decision structures: can make a decision based only on the current inputs: gates belong to this category.
 - Storage structures: permit the storage of information (as bits).
- Combinational logic circuits
 - a combinational logic structure is constructed from decision elements only: i.e. simple gates or other combinational logic circuits.
 - its output depends solely on its current input.
- Sequential logic circuits
 - combine combinational circuits & storage devices - we'll deal with these shortly.
- Four examples of combinational logic circuits
 - Decoder
 - Multiplexer (MUX)
 - Full adder
 - **Programmable Logic Array**

Decoder

 


- An n input decoder has 2^n outputs.
- Output $_i$ is 1 iff the binary value of the n -bit input is i .
- At any time, exactly one output is 1, all others are 0.

Multiplexer (MUX)

- In general, a MUX has
 - 2^n data inputs
 - n select (or control) lines
 - and 1 output.
- It behaves like a channel selector.
 
$$\text{Out} = A \cdot \bar{S}_0 \cdot \bar{S}_1 + B \cdot \bar{S}_0 \cdot S_1 + C \cdot S_0 \cdot \bar{S}_1 + D \cdot S_0 \cdot S_1$$



A 4-to-1 MUX: Out takes the value of A,B, C or D, depending on the value of S (00, 01, 10, 11)

Adder

•Half Adder

- 2 inputs
- 2 outputs: sum and carry

a_i	b_i	c_{i+1}	s_i
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Half-adder truth table

•Full Adder

- performs the addition in column i
- 3 inputs: a_i , b_i and c_i
- 2 outputs: s_i and c_{i+1}
- c_i is the carry in from bit position $i-1$
- c_{i+1} is the carry out to bit position $i+1$

$$\begin{array}{r}
 a_{n-1} \ a_{n-2} \ \dots \ a_1 \ a_0 \\
 + \ b_{n-1} \ b_{n-2} \ \dots \ b_1 \ b_0 \\
 + \ c_{n-1} \ c_{n-2} \ \dots \ c_1 \ 0 \\
 \hline
 s_{n-1} \ s_{n-2} \ \dots \ s_1 \ s_0
 \end{array}$$

Gate Level Full Adder

A_i	B_i	C_i	C_{i+1}	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


Figure 3.15: Gate Level Description of a Full Adder.

Full Adder - Expressions

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i . b_i + c_i . (a_i + b_i)$$

where


\oplus is exclusive OR

$.$ is the AND operation

$+$ is the OR operation

- verify that this corresponds to the gate-level implementation.

A 4-bit Ripple-Carry Adder

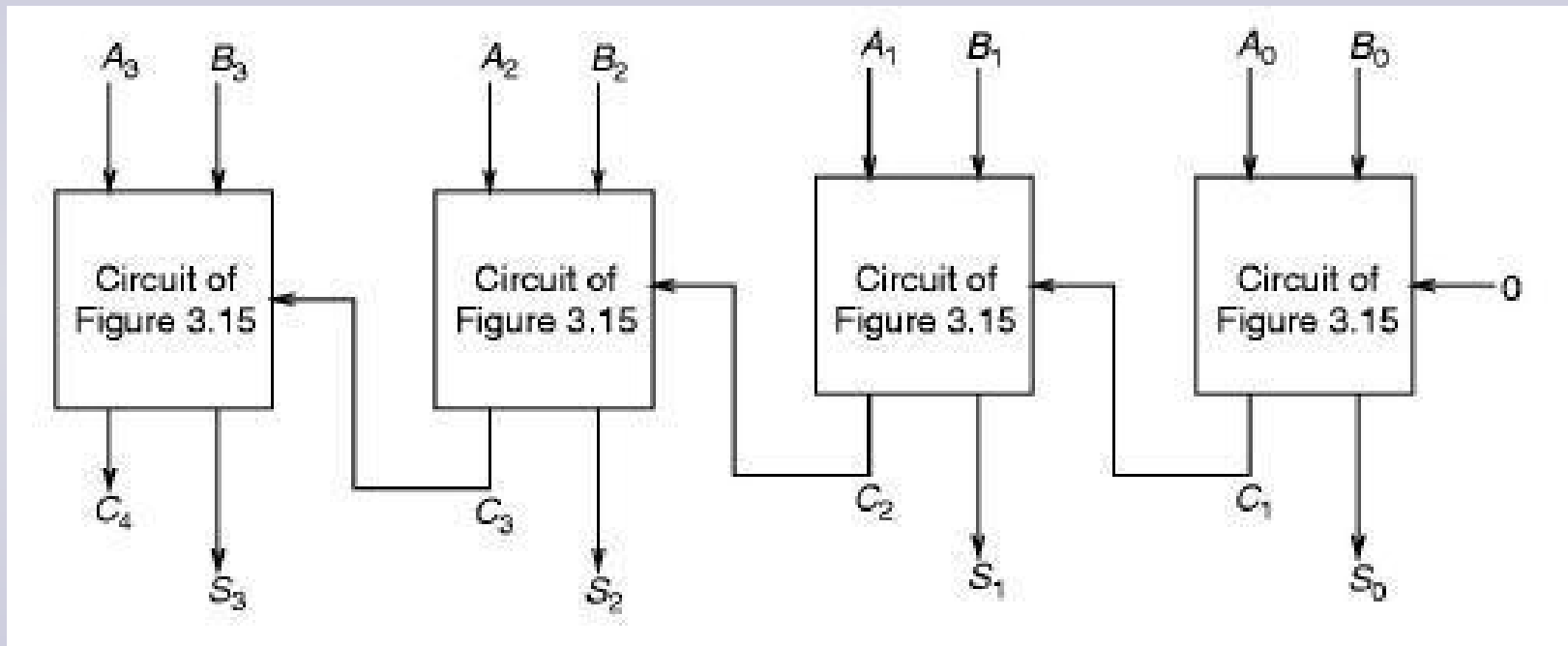

Carry Lookahead Addition

- We can pre-compute the carry

- The carry in bit 4 (C_4) is 1 if any two of A_3 , B_3 or C_3 are 1.

$$\begin{aligned}C_4 &= A_3B_3 + C_3A_3 + C_3B_3 \\&= A_3 \cdot B_3 + C_3(A_3 + B_3) \\&= G_3 + P_3C_3\end{aligned}$$


- P_3 is called the propagate bit, and G_3 the generate bit

$$\begin{aligned}C_4 &= G_3 + P_3C_3 = G_3 + P_3(G_2 + P_2C_2) = G_3 + P_3(G_2 + P_2(G_1 + P_1C_1)) \\&= \dots = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1C_0\end{aligned}$$



- So every carry bit can be pre-computed using all the previous inputs.
- Pre-computation can be done in 2 gate delays.

Programmable Logic Array

 - It is possible to build a logic circuit that uses logic circuits to decide what logic circuits to implement!




Storage Elements: R-S Latch

  

- The output *a* of the R-S latch can be set to 1 by momentarily setting S to 0 while keeping R at 1.
- Conversely, the output *a* can be set to 0 by keeping S at 1 and momentarily setting R to 0.
- When S is set back to 1 the output *a* stays at 1.
- When R is set back to 1, the output *a* stays at 0.


The flip-flop (R-S latch) is a bi-stable element

Storage Elements: Gated D Latch

 

- The gated D latch is an extension of the R-S latch
- Two inputs: data (*D*) and write enable (*WE*)
- When the *WE* (write enable) is set to 1, the output of the latch is set to the value of *D*.
- The output is held until *WE* is “asserted” (set to 1) again.

Registers

 

A 4-bit register made of four D latches

Memory - 1

A large number of addressable fixed size locations

• Address Space

n bits allow the addressing of **2^n** memory locations.

- Example: 24 bits can address $2^{24} = 16,777,216$ locations (i.e. 16M locations).
- If each location holds 1 byte (= 8 bits) then the memory is 16MB.
- If each location holds one word (32 bits = 4 bytes) then it is 64 MB.

Memory - 2

• Addressability

- Computers are either **byte** or **word** addressable - i.e. each memory location holds either 8 bits (1 byte), or a full standard word for that computer (16 bits for the LC-3, more typically 32 bits, though now many machines use 64 bit words).
- Normally, a whole word is written and read at a time:
 - *If the computer is **word** addressable, this is simply a single address location.*
 - *If the computer is **byte** addressable, and uses a multi-byte word, then the word address is conventionally either that of its most significant byte (big endian machines) or of its least significant byte (little endian machines).*

Building a Memory

- **Each bit**


- is a gated D-latch

- **Each location**

- consists of w bits (here $w = 1$)
 - $w = 8$ if the memory is byte addressable

- **Addressing**

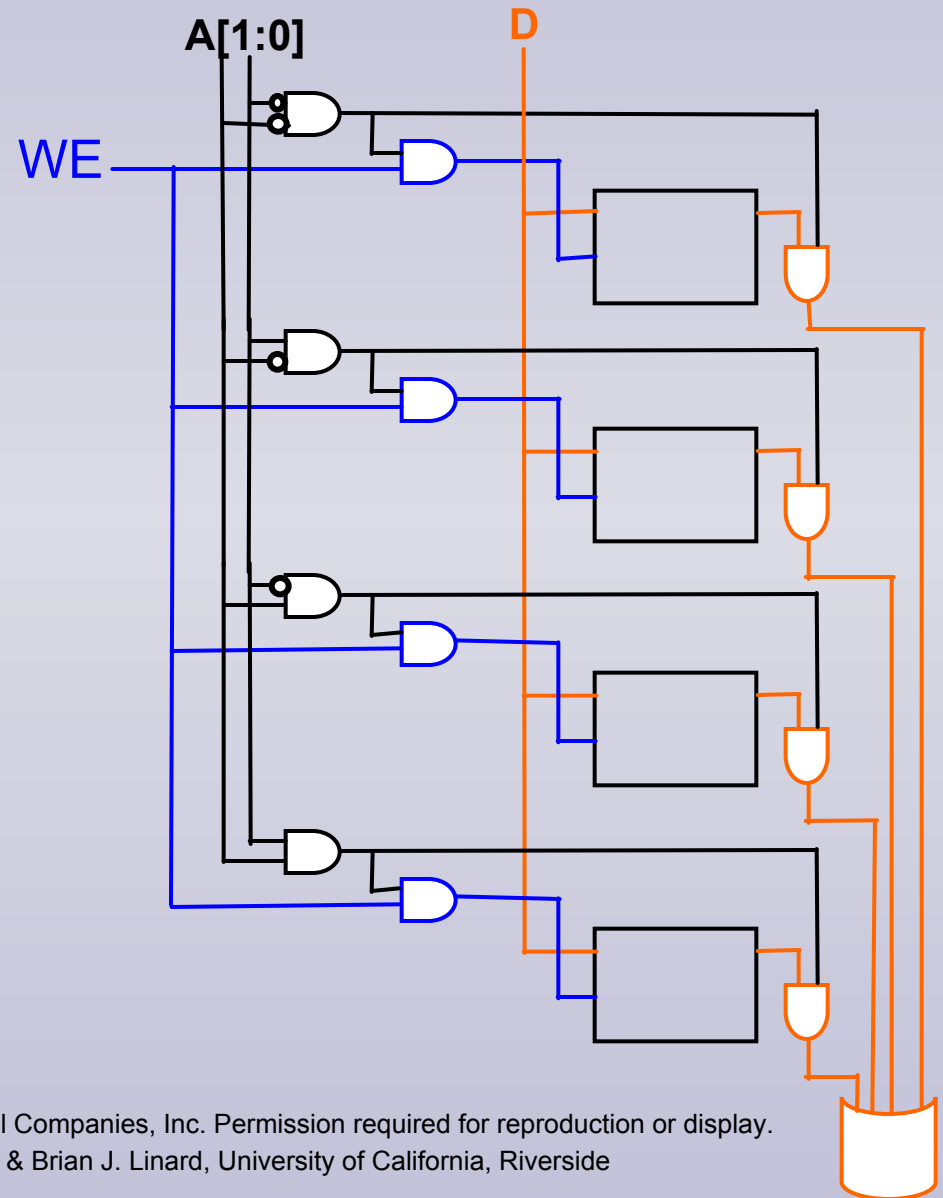- n locations means $\log_2 n$ address bits (here 2 bits \Rightarrow 4 locations)
 - decoder circuit translates address into 1 of n locations




Memory Example


A 2^2 by 3 bits memory:

- two address lines: A[1:0]
- three data lines: D[2:0]
- one control line: WE

One gated
D-latch

 


Reading a location in memory

 

Using Memory Building Blocks

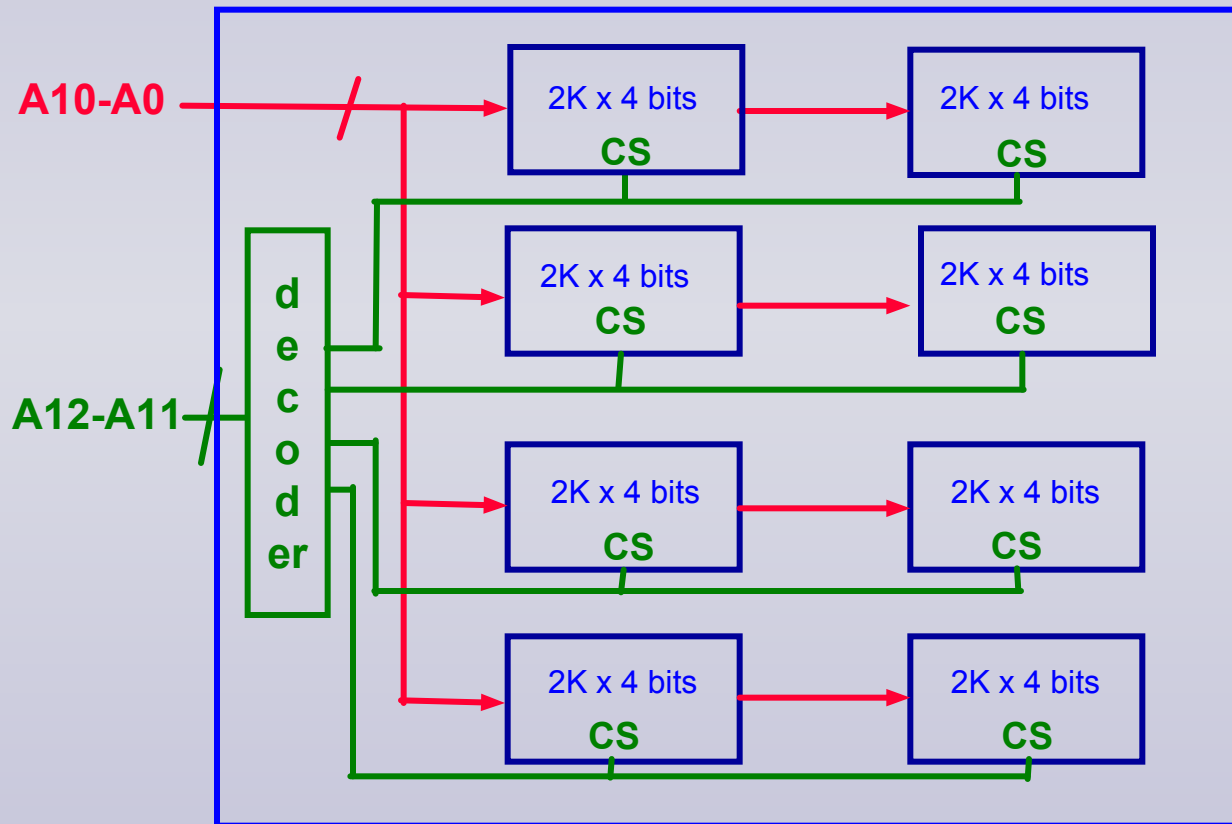- Building an 8K byte memory using chips that are 2K by 4 bits.




- CS = chip select:
when set, it enables
the addressing,
reading and writing
of that chip.

This is an 8KB
byte addressable
memory

Memory One Word Wide

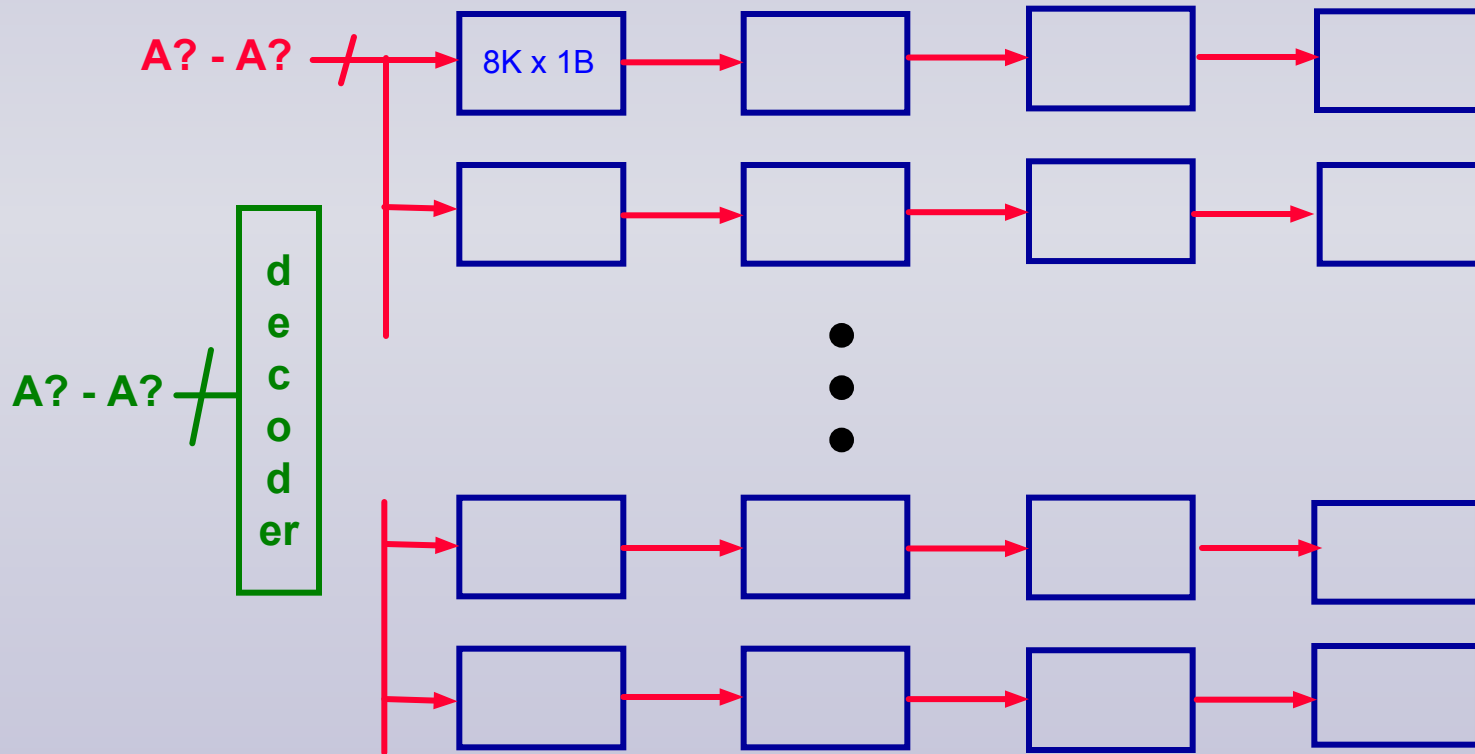- Use the previous memory block of 8K x 1 byte to build a memory that is 64K words, with each location one word of 32 bits.
 - ◆ what are the address lines if the memory is word addressed? or byte addressed?




Sequential Logic Circuits - 1

- **The concept of state**

- the state of a system is a “snapshot” of all relevant elements at a moment in time.
- a given system will often have only a finite number of possible states.
- e.g. the game of tic-tac-toe has only a certain number of possible dispositions of Xs and Os on the 3x3 grid.
- A given game of tic-tac-toe will progress through a subset of these possible states (until someone wins) - i.e. it traverses a specific path through “state space”, one move at a time.
- For many systems, we can define the rule which determine under what conditions a system can move from one state to another.

Sequential Logic Circuits - 2

 


- The output is a function of the current input and the previous state
- It is computed by the *combinational logic circuit*
- The state is stored in the *storage element*
- The new state is also a function of the previous state and the current input
- This can work only if we make transitions from one state to another at well-defined times - this is why they are called sequential circuits.



Finite State Machines

- **Many systems meet the following five conditions:**
 - A finite number of states
 - A finite number of external inputs
 - A finite number of external outputs
 - An explicit specification of all allowed state transitions
 - An explicit specification of the rules for each external output value
- **In fact, as we will see, a microprocessor is a perfect candidate for description as a FSM.**

Finite State Machine Example - 1

 

  - Three groups of lights to be lit in a sequence: group 1 on, groups 1 & 2 on, all groups on, all off.
- The lights are on only if the main switch is on.
- Four states: so we need two bits to identify each state.



Finite State Machine Example - 2

- **When is group 1 on?**



- in states 01, 10 and 11 - but only when the switch is on!

- can you come up with a logic expression for d_0 and d_1 ?

- **When do we switch to the next state?**


- the two bits of $d[1:0]$ are updated at every clock cycle
- we have to make sure that the new state does not propagate to the combinational circuit input until the next clock cycle.

Finite State Machine Example - 3

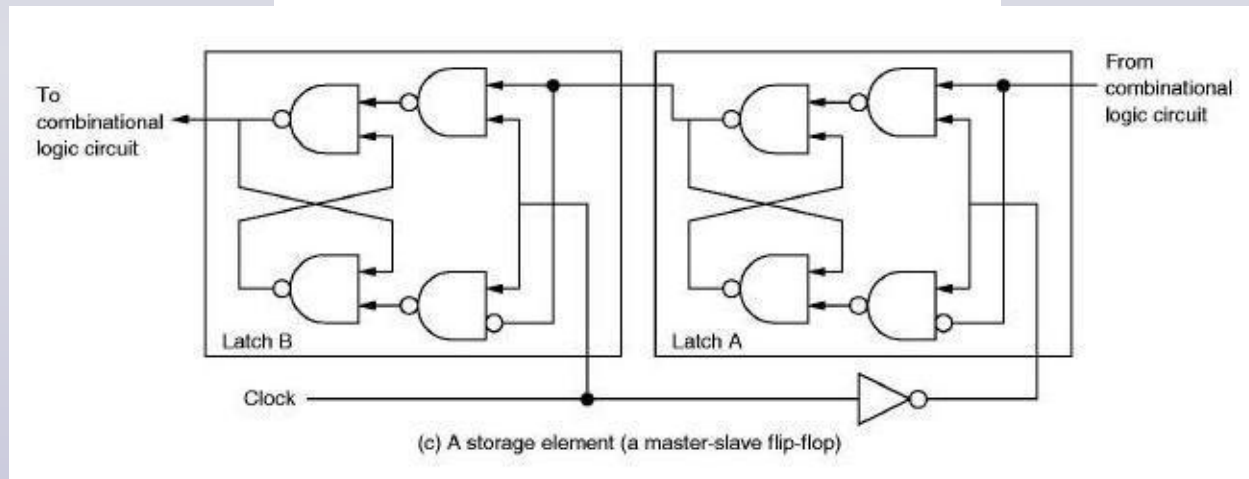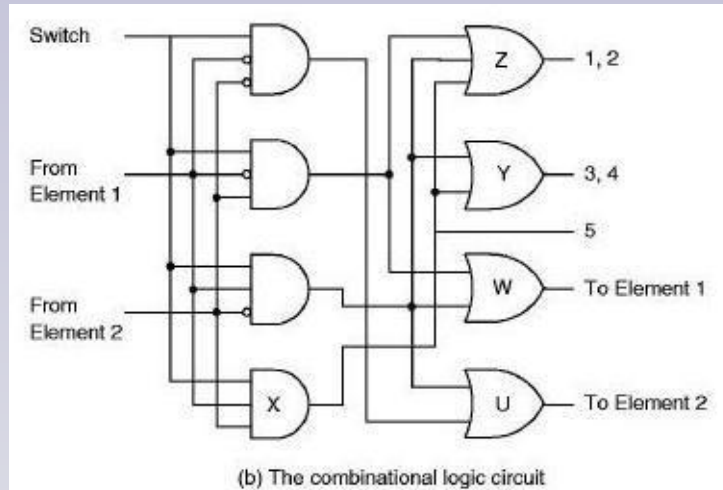

Note that signal “1,2” corresponds to “out1”; “3,4” to out2; “5” to out3; and Element 1 to d_1 , Element 2 to d_0

The LC-3 as a Finite State Machine

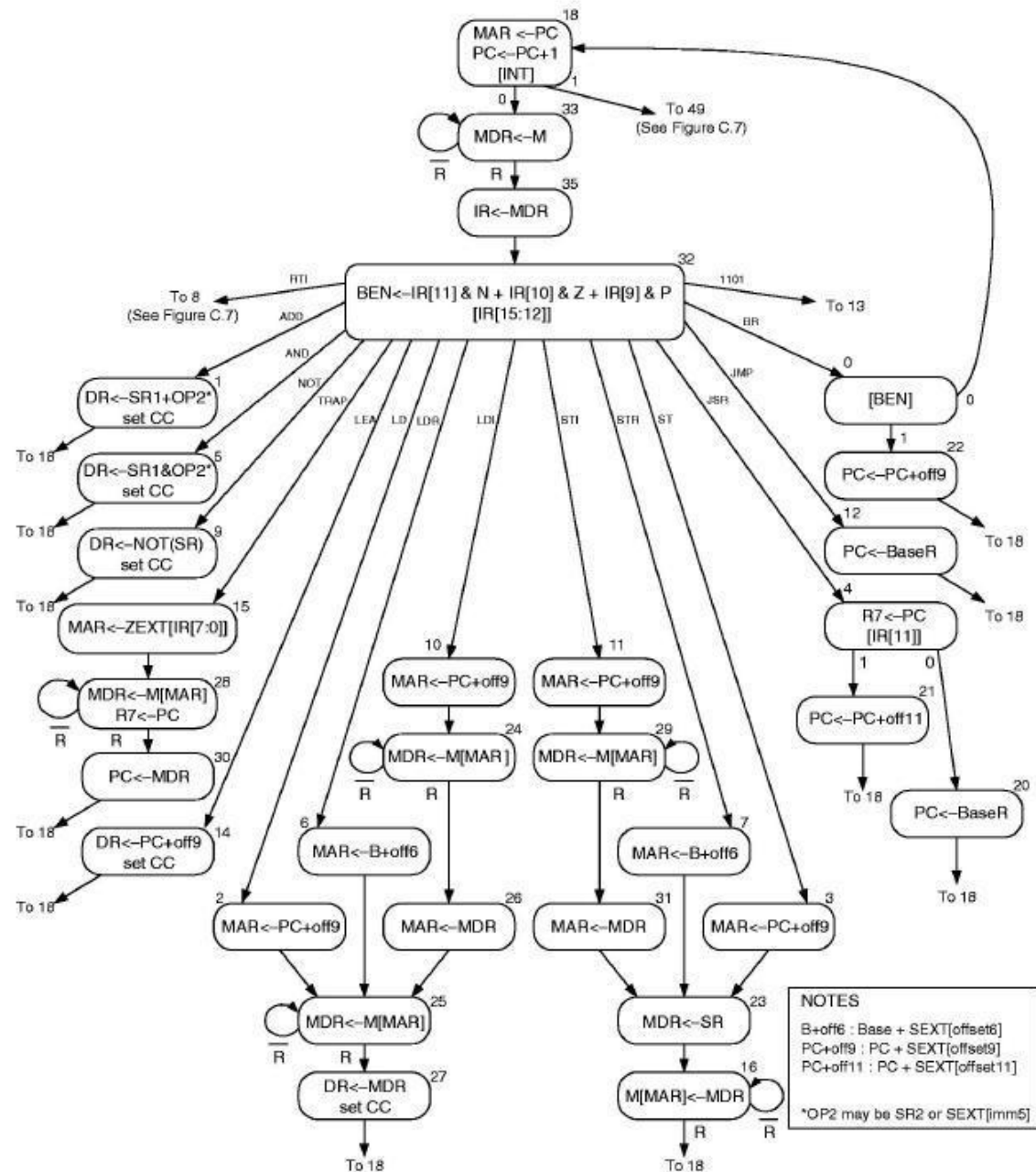

Data Path of the LC-3

